

Old QUIZ 3:

Design a square wave generator whose frequency is either 100 Hz or 10 Hz. As selected by a selector switch: